

Implementation of Gate ques over Arduino

Aditya Gupta


Contents

1	Problem	2
2	Introduction	2
3	Components	2
4	Solution	3
4.1	Karnaugh Map	3
4.2	Truth Table	3
5	Connections	4
5.1	LED to Arduino	4
5.2	Input Pins to Arduino	4
5.3	Setting Input Pin Values	4
5.4	Repository	4

1 Problem

(GATE IN-2022 Ques 21)

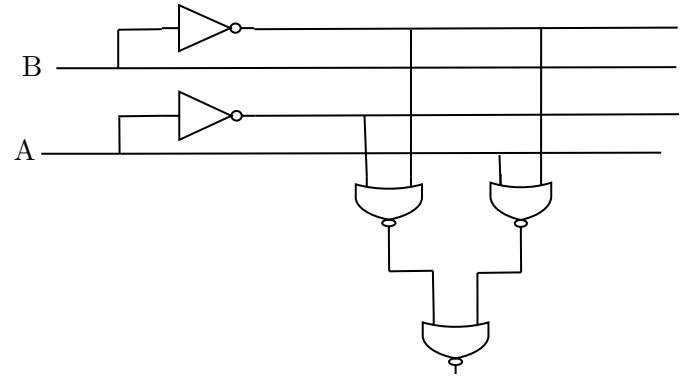Q.22 The logic block shown has an output F:



2 Introduction

For a given set of Boolean Logic Inputs, we can define the following terms:

- **Minterm** is a boolean expression resulting in an output of 1 for the minimum number of cells in a Karnaugh-Map (K-Map) and 0 in other cells.
- **Sum of Products** is a boolean expression for the *Sum* (OR) of various *Product* (AND) terms.
- **'do not care'** terms for a boolean expression are the set of input values for which the output of the function does not matter. The value for these can be taken as 0 or 1 by choice

3 Components

Component	Value	Quantity
Arduino	UNO	1
Breadboard	-	1
LED	-	1
Jumper Wires	M-M	10
Resistor	220 Ω	1

Table 1: Table of Components

4 Solution

4.1 Karnaugh Map

		B	
		0	1
A	0	1	0
	1	1	0

The final expression is of output is $Y = F(!B)$

Logic for the code will be $Y = !B$

4.2 Truth Table

A	B	C
0	0	1
0	1	0
1	0	1
1	1	0

5 Connections

5.1 LED to Arduino

LED connections to Arduino are as follows:

Arduino	5	GND
LED	+	-

Table 2: LED Connections

5.2 Input Pins to Arduino

Input Pin Connections to Arduino are as follows:

Arduino	D2	D3
Term	A	B

Table 3: Input Pin Connections

5.3 Setting Input Pin Values

The values of the Input pins are taken by connecting them to either 5V or GND according to Truth Table

5.4 Repository

Code is also available online at the following repository:

<https://github.com/Aditya2004-hue/LATEX/blob/main/codes/gate.ino>